

- (b) Draw the block diagram of CRO and explain the function of each block in detail. 10

**SECTION – D**

8. What is LED ? Discuss its principle, construction, working, advantages and disadvantages. Also make comparison between LED and LCD. 20
9. (a) Make a comparison between dynamic scattering and field effect LCD displays. 10
- (b) Write short note on fourteen segment display. 10

Roll No. ....

**24004**

**B. Tech. 2nd Semester  
(Common for all Branches)  
Examination – May, 2017**

**BASICS OF ELECTRONICS**

**Paper : ECE-101-F**

**Time : Three Hours ]**

**[ Maximum Marks : 100**

Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.

**Note :** Attempt *five* questions in all, selecting *one* question from each Section. Question No. 1 is *compulsory*. All questions carry equal marks.

1. (a) What is an ideal diode ? 2
- (b) Give definition of forbidden energy gap and knee voltage. 4
- (c) Define common mode rejection ratio. 3

- (d) What is the main difference between amplifier and oscillator ? 2
- (e) Discuss the drawback of S-R flip-flop. 2
- (f) Write about basic logic gates. 3
- (g) Why LED emits light of different colours. 2
- (h) Define dot matrix display. 2

### SECTION – A

- 2. (a) What is PN junction diode ? Draw and explain its terminal characteristics. 10
- (b) Make a comparison between the following : 10
  - (i) Intrinsic and extrinsic semiconductors.
  - (ii) Drift and diffusion currents.
- 3. (a) Draw the circuit of an R-C coupled amplifier. Draw its gain versus frequency characteristics and indicate cutoff frequency and bandwidth. 10
- (b) An amplifier with a negative feedback provides an output voltage of 5 V with an input voltage of 0.2 V. On removal of feedback, it needs only 0.1 V input to give the same output. Determine :
  - (i) Gain without feedback.

(ii) Gain with feedback.

(iii) Feedback ratio. 10

### SECTION – B

- 4. (a) Describe the principle of operation of a Wein bridge oscillator and give the condition for sustained oscillation. 10
- (b) Explain use of Op-Amp as a summing, scaling, and average amplifier. 10
- 5. (a) Draw the pin diagram of IC 741 used as an Op-Amp and explain the function of each pin. 10
- (b) Write a short notes on voltage regulator. 10

### SECTION – C

- 6. (a) Realize EX-OR gate using four NAND gates only. 10
- (b) Draw and explain the circuit diagram of J-K flip-flop. Give its truth table also. 10
- 7. (a) Make a comparison between combinational and sequential circuits. 10