

Roll No.

2004

B. E. 3rd Sem. (ECE)

Examination – December, 2013

NETWORK THEORY

'E' Scheme

Paper : EE-203-E


Time : Three hours]

[Maximum Marks : 100

Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.

Note : Attempt any *five* out of eight questions.

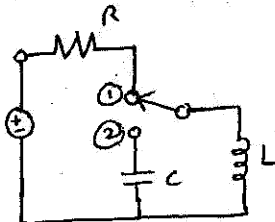1. (a) Describe the transient response of R-C kct with impulse function. 10
- (b) In the kct of figure, steady state exists when switch K is in position 1, At $t = 0$, it moved to position (2). Obtain the expression for current using L. T. : 10




2. (a) Derive z-parameters in terms of T-parameter. 10

(b) Explain series-series connection for two port n/w with neat ckt diagram. 10

3. Define Transfer Function. Can we define transfer function for one port n/w ? Explain with reason. Also write all possible transfer functions & inverse transfer functions. 20

4. (a) Define tree, forest, graph, oriented graph and connected graph with examples. 10

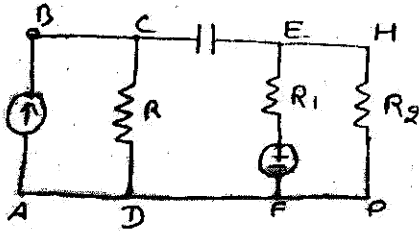(b) For given ckt, draw graph & prepare Cut set matrix & Tie set matrix. 10



5. (a) State the properties of real functions. 10

(b). Define Hurwitz polynomial and also write its properties. 10

6. An impedance function is given by : 20

$$Z(s) = \frac{(s+2)(s+9)}{s(s+4)(s+5)}$$

Find R-C representation using foster (1), foster (2) & cauer (1), cauer (2).

7. (a) $F(s) = \frac{s^2 + s + 6}{s^2 + s + 1}$ check for P. R. function. 10

(b) Explain properties of R. C. impedances.

8. Write short notes on : 20

(a) Low pass filter.

(b) Restrictions on pole zero locations for transfer functions.