

24025

B.Tech. 3rd Semester AEIE F-Scheme Examination,

December-2014

NETWORK THEORY

Paper-EE-203-F

Time allowed : 3 hours] [Maximum marks : 100

Note : Attempt five questions in total selecting one questions from each section. Question No. 1 is compulsory.


1. (i) Define signal ? Draw the waveform of $F(t) = [u(t) - u(t - 1)]$
- (ii) Explain the condition of Hurwitz.
- (iii) What are the properties of RC driving point immittance ?
- (iv) Derive the expression for synthesis of Y_{21} and Z_{21} with 1 ohm termination. 20

Section-A

2. (a) In series RLC ckt. Having data is $R = 1/16$ ohm, $L = 1/16$ H, $C = 4$ F determine $V(0+)$ $dV(0+)/dt$ and $d^2V(0+)/dt^2$ (14)

(2)


24025

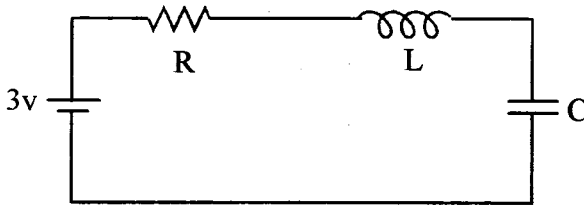

- (b) Derive the expression for transient response in AC for RL series. (6)
3. (a) Explain the concept of complex frequency. (10)
- (b) Explain the initial value theorem. (10)

Section-B

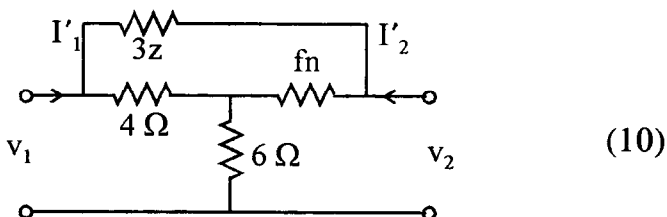4. (a) The two port network A and B are connected in parallel if the input voltage is 2V and current is 2A, 3A gets the output as 10V, 5A, 1A, calculate the parameter. (10)
- (b) Find the Y-parameter of the ckt. Given below.




24025

(3)

24025

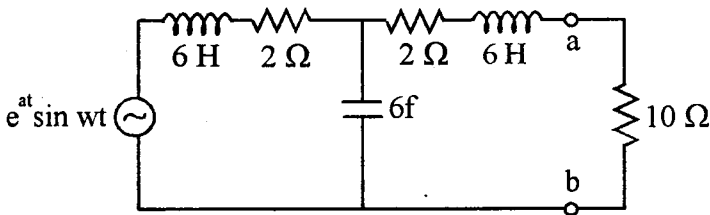5. (a) Apply Norton's theorem using Laplace transform for the ckt. Given below across a and b. (10)



- (b) Explain the parallel-series connection of two port network. (10)

Section-C

6. (a) Check whether the given function are p.r.f or not

$$f(s) = (s^3 + 5s^2 + 9s + 3) / (s^3 + 4s^2 + 7s + 9) \quad (8)$$

- (b) Check whether the given polynomial are Hurwitz or not.

$$P(s) = s^4 + s^3 + 2s^2 + 3s + 2$$

$$z(s) = \frac{(s^2 + 4s + 1)}{4s^2 + 5s + 1} \quad (12)$$

7. Realize


(i) Cauer – II

(ii) Foster – II

(20)

Section–D

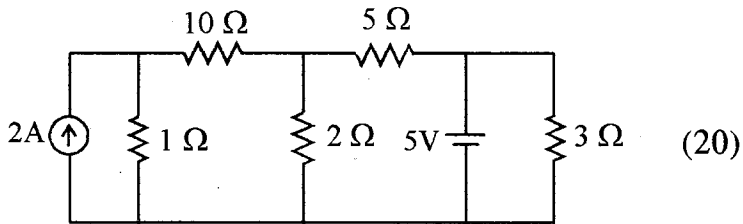8. Draw the oriented graph of the network as shown in figure. Determine the fundamental loop cutset matrix.



9. Synthesise the Z_{21} and Y_{21} as shown in the polynomial given below :

$$Z'_{21} = \frac{1}{s^4 + 3s^3 + 2s^2 + 6s + 5}$$

$$Y'_{21} = \frac{1}{s^3 + 3s^2 + 2s + 6}$$

20